



$$\begin{cases} V_{out} = -A V_- \\ i_p = i_1 + i_2 \\ i_1 = V_- \cdot i\omega C_j \\ i_2 = -V_{out} / R_f \end{cases}$$

$$\Rightarrow V_{out} = -A \frac{i_1}{i\omega C_j} = \frac{-A}{i\omega C_j} (i_p - i_2)$$

$$= \frac{-A}{i\omega C_j} (i_p + V_{out} / R_f)$$

$$\left(1 + \frac{A}{i\omega C_j R_f}\right) V_{out} = \frac{-A}{i\omega C_j} i_p$$

$$R_{TRANS} \equiv \frac{-V_{out}}{i_p} = R_f \frac{1}{1 + i\omega C_j R_f / A}$$

$$= R_f \frac{1}{1 + i f / f_c} \quad f_c = \frac{A}{2\pi C_j R_f}$$

1) As far as $A \gg f/f_1$ $R_{TRANS} = R_f$

2) if $A \ll f/f_1$ $R_{TRANS} = R_f \times \frac{A f_1}{i f}$

3) at $A = f/f_1$ oscillation

$$\left(= R_f \frac{1}{1 + i f / (A f_1)} \right) \equiv A f_1$$

Assume $A = A_0 \frac{1}{1 + i f / f_A}$, $R_{TRANS} = \frac{R_f}{1 + i \frac{f}{f_1 A_0} - \frac{f^2}{f_1 f_A A_0}}$

$$f_{cut} = \sqrt{f_1 f_A A_0} \quad (= \sqrt{f_1 \times GBW})$$

$$Q = \sqrt{\frac{f_A A_0}{f_1}}$$